




Unit1 Lecture 1 MUX Demux Encoder Decoder

Computer Organisation and Design (Lovely Professional University)

THE HALF ADDER :-

→ Logic symbol is

 


→ Half Adder truth table is

A	B	Σ	Cout
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$\Sigma = \bar{A}B + A\bar{B} \\ = A \oplus B$$


$$C_{out} = AB$$

→ Half Adder logic diagram is

 

THE FULL ADDER :-

→ Logic symbol for Full Adder is

 

→ Full Adder truth table is

A	B	Cin	Σ	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$\begin{aligned} \Sigma &= \bar{A}\bar{B}C_{in} + \bar{A}B\bar{C}_{in} + A\bar{B}\bar{C}_{in} + ABC_{in} \\ &= C_{in}(\bar{A}\bar{B} + AB) + \bar{C}_{in}(\bar{A}B + A\bar{B}) \\ &= C_{in}(\overline{A \oplus B}) + \bar{C}_{in}(A \oplus B) \\ &= A \oplus B \oplus C_{in} \end{aligned}$$


$$\begin{aligned} C_{out} &= \bar{A}BC_{in} + A\bar{B}C_{in} + AB\bar{C}_{in} + ABC_{in} \\ &= (\bar{A}B + A\bar{B})C_{in} + AB(\bar{C}_{in} + C_{in}) \\ &= (A \oplus B)C_{in} + AB \end{aligned}$$

$$\therefore \Sigma = A \oplus B \oplus C_{in}$$

$$C_{out} = AB + (A \oplus B)C_{in}$$

→ Full Adder logic diagram is.

(2)

 


$$\Sigma = A \oplus B \oplus C_{in}$$

$$C_{out} = AB + C_{in}(A \oplus B)$$

THE HALF SUBTRACTOR :-

→ Logic Symbol is

 


→ Half subtractor truth table is

A	B	d	b
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

$$d = \bar{A}B + A\bar{B} = A \oplus B$$


$$b = \bar{A}B$$

→ Half subtractor logic diagram is

 

→ THE FULL SUBTRACTOR :-

→ Logic Symbol for Full subtractor is

 

→ Full subtractor truth table is

A	B	bin	d	b
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

$$d = \bar{A}\bar{B}b_{in} + \bar{A}B\bar{b}_{in} + A\bar{B}\bar{b}_{in} + ABb_{in}$$


$$= (\bar{A}\bar{B} + AB)b_{in} + (\bar{A}B + A\bar{B})\bar{b}_{in}$$

$$= (A \oplus B)b_{in} + (A \oplus B)\bar{b}_{in}$$

$$= A \oplus B \oplus b_{in}$$

$$\begin{aligned}
 b &= \bar{A}\bar{B}b_{in} + \bar{A}B\bar{b}_{in} + \bar{A}Bb_{in} + ABb_{in} \\
 &= (\bar{A}\bar{B} + AB)b_{in} + \bar{A}B(\bar{b}_{in} + b_{in}) \\
 &= (\bar{A} \oplus B)b_{in} + \bar{A}B
 \end{aligned}$$

→ Full subtractor logic diagram is

 

PARITY BIT GENERATOR :-

i) Design of an even parity bit generator for a 4-bit input :-


4-bit data input				output parity bit (F)
A	B	C	D	
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

$$F = \sum m(1, 2, 4, 7, 8, 11, 13, 14)$$

	CD=00	CD=01	CD=11	CD=10
AB=00	0	1	0	1
AB=01	1	0	1	0
AB=11	0	1	0	1
AB=10	1	0	1	0

Chess board configuration.
 
$$\therefore F = A \oplus B \oplus C \oplus D$$



Logic circuit diagram for even parity generator ↗


⇒ Design of an odd parity bit generator for a 4-bit input

A	B	C	D	F
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

$$F = \sum m(0, 3, 5, 6, 9, 10, 12, 15)$$

AB \ CD	00	01	11	10
00	1		1	2
01		4	5	6
11	12	13	15	14
10	8	9	11	10

 
$$F = \overline{A \oplus B \oplus C \oplus D}$$



Logic circuit diagram for odd bit Parity generator.


⇒ Even parity bit checker & odd parity bit checker.

 → At the receiving end, if the word received has an even number of 1s in odd parity system (or) an odd number of 1s in even parity system, it implies that an error occurred.



Even parity bit checker

 If we get Error (0) then no error occurred P(0). Error(1) then error occurred.



odd parity bit checker

If we get error(1) then no error occurred. P(0) ... Error(0) then error occurred.

1-bit Magnitude Comparator:- (A, B are input bits, E, G, L are o/p bits) (5)

$$\rightarrow \text{If } A=B \Rightarrow E=A \odot B$$


If $A = B \Rightarrow E = 1$

→ If $A > B$: $G_1 = A\bar{B}$ (or)

$$A > B \Rightarrow G_1 = 1$$
$$A < B \quad \Rightarrow L = 1.$$

→ If $A < B$: $\neg L = \bar{A}B$.

 → Logic circuit diagram for 1-bit magnitude comparator is given by



→ Truth table for 1-bit magnitude comparator is given by.

A	B	L	E	G
0	0	0	1	0
0	1	1	0	0
1	0	0	0	1
1	1	0	1	0

⇒ ENCODER :-

→ ENCODER :-
→ An Encoder is a device which converts familiar numbers or symbols into coded format.


→ It is a combinational CKT that performs the reverse operation of decoder

→ It is used to minimize the data lines.

→ out of n inputs, if every time only single input is high, then there is no need to use n inputs, then we can represent same information in output in m bits or m outputs. ($m < n$).

→ Relation between n & m is $n = 2^m$ ($n = \text{no. of input lines}$)
($m = \text{no. of output lines}$).

→

 

n - inputs
m - outputs.
 $n > m$.

Encoder.

⇒ octal to Binary Encoder :- (8-line to 3-line encoder).

→ Truth table is given as.

Octal digits		Binary		
		A_2	A_1	A_0
D_0	0	0	0	0
D_1	1	0	0	1
D_2	2	0	1	0
D_3	3	0	1	1
D_4	4	1	0	0
D_5	5	1	0	1
D_6	6	1	1	0
D_7	7	1	1	1

$$A_2 = 4 + 5 + 6 + 7$$

$$= D_4 + D_5 + D_6 + D_7$$


$$A_1 = 2 + 3 + 6 + 7$$

$$= D_2 + D_3 + D_6 + D_7$$

$$A_0 = 1 + 3 + 5 + 7$$


$$= D_1 + D_3 + D_5 + D_7$$

 → Logic diagram for octal - binary encoder is given by.



✓
(write this in exam)

(or)

 

Decimal -to- BCD ENCODER :-

→ Truth table is given by

Decimal inputs		Binary			
		A ₃	A ₂	A ₁	A ₀
D ₀	0	0	0	0	0
D ₁	1	0	0	0	1
D ₂	2	0	0	1	0
D ₃	3	0	0	1	1
D ₄	4	0	1	0	0
D ₅	5	0	1	0	1
D ₆	6	0	1	1	0
D ₇	7	0	1	1	1
D ₈	8	1	0	0	0
D ₉	9	1	0	0	1

$$A_0 = 1 + 3 + 5 + 7 + 9$$


$$= D_1 + D_3 + D_5 + D_7 + D_9$$

$$A_1 = 2 + 3 + 6 + 7$$

$$= D_2 + D_3 + D_6 + D_7$$

$$A_2 = D_4 + D_5 + D_6 + D_7$$


$$A_3 = D_8 + D_9$$

 

Logic diagram for DEC-BCD ENCODER.


⇒ Decoder :-

 → A decoder is a logic circuit that converts n-bit binary input code into M output lines such that only one output line is activated for each one of the possible combinations of input.




In Decoder, Enable is also present.
(Active low & Active high).

→ 2-Line-to-4-Line Decoder :-

 


Inputs		Outputs			
A	B	D ₀	D ₁	D ₂	D ₃
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

 


→ Truth-table with Active high enable

E	A	B	D ₀	D ₁	D ₂	D ₃
0	x	x	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

 

→ Truth-table with Active ^{Low} enable with NAND gates.


E	A	B	D ₀	D ₁	D ₂	D ₃
1	x	x	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

 

⇒ 3-Line-to-8 Line decoder:-

Inputs			Outputs							
A	B	C	D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

 Truth-table (with No enable & Active high enable)



LOGIC DIAGRAM.


* Implement the following Boolean function with Decoder.

9

$$Y(A, B, C) = \sum m(0, 1, 2, 4, 6, 7)$$

Sol:- Truth table is

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

 


* Implement or Design a Full Adder using Decoder.

Sol:- Truth table for Full Adder is

A	B	Cin	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$\text{SUM} = \sum m(1, 2, 4, 7)$$

$$\text{Carry} = \sum m(3, 5, 6, 7)$$

 


Multiplexer :- (Data selector)

→ It is a combinational circuit that selects binary information from one of many input lines and directs it to o/p line.

→ It is simply a Data selector.

→ It has $2^m = n$ inputs and one output and m selection lines. ($2^m:1$)


→ Logic symbol for multiplexer is

 

→ Multiplexer shortly known as MUX.

⇒ 2:1 MUX :-

→ Logic symbol for 2:1 MUX is

 


Truth table for 2:1 MUX is


E	S	Y
0	X	0
1	0	I_0
1	1	I_1

→ Logic function of 2:1 MUX is $Y = E(\bar{S}I_0 + SI_1)$

→ Logic circuit diagram is given by

 


→ If we neglect Enable,

 

4:1 MUX :-

→ logic symbol

 


↓ Logic function

$$Y = \bar{S}_1 \bar{S}_0 I_0 + \bar{S}_1 S_0 I_1 + S_1 \bar{S}_0 I_2 + S_1 S_0 I_3$$

Truth table is given by

S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

→

 

$$Y = \bar{S}_1 \bar{S}_0 I_0 + \bar{S}_1 S_0 I_1 + S_1 \bar{S}_0 I_2 + S_1 S_0 I_3$$

8:1 MUX :-


→ Apply same above method, you will get 8:1 MUX also.

⇒ Design of Boolean function using Multiplexer (4:1 & 8:1 MUX)

* Implement or Design $Y(A, B, C) = \sum m(0, 2, 4, 6, 7)$ using 8:1 MUX.

Sol:- Truth table of $Y(A, B, C)$ is

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1


 


+Vcc means 1
GND means 0.



* Implement or Design $Y(A, B, C) = \sum m(0, 2, 4, 6, 7)$ using 4:1 MUX.

Sol:- Truth table is

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

  

If we take AB as selection lines,

  



* Implement or Design Full Adder using 4:1 MUX.

→ Truth table of Full Adder is







A	B	Cin	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$\text{SUM} = \sum m(1, 2, 4, 7)$$

$$\text{Carry} = \sum m(3, 5, 6, 7)$$

  


If B, Cin are selection lines then

      


⇒ DEMULTIPLEXER :- (Data Distributor)

 
- 1 input and many outputs. ($1:2^m$)
- Reverse operation of Multiplexer.
- Data Distributor




i) 1:2 DEMUX :-

 


E	S ₀	Y ₀	Y ₁
0	x	0	0
1	0	I	0
1	1	0	I

 


ii) 1:4 DEMUX :-

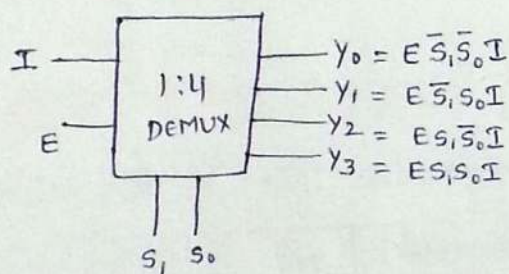

E	S ₁	S ₀	Y ₀	Y ₁	Y ₂	Y ₃
0	x	x	0	0	0	0
1	0	0	I	0	0	0
1	0	1	0	I	0	0
1	1	0	0	0	I	0
1	1	1	0	0	0	I

 

⇒ Demultiplexer as a Decoder :-

 

DEMUX TRUTH TABLE

S_1	S_0	Y_0	Y_1	Y_2	Y_3
0	0	I	0	0	0
0	1	0	I	0	0
1	0	0	0	I	0
1	1	0	0	0	I

I_1	I_0	Y_0	Y_1	Y_2	Y_3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

* In demux, if Input (I) = 1 and $S_1 = I_1$ and $S_0 = I_0$ then DEMUX act as Decoder.


* Design a Full Subtractor using 1:8 DEMUX

Truth table of Full Subtractor is given as

A	B	Bin	Difference	Borrow
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

$$\text{Difference} = \sum m(1, 2, 4, 7)$$


$$\text{Borrow} = \sum m(1, 2, 3, 7)$$

 

* Design a Boolean expression $Y(A, B, C) = AB + C$ Using 1:8 DEMUX. (15)


Sol:-
 
$$\begin{aligned}
 Y(A, B, C) &= AB + C \\
 &= AB(C + \bar{C}) + C(A + \bar{A})(B + \bar{B}) \\
 &= ABC + AB\bar{C} + (AC + \bar{A}C)(B + \bar{B}) \\
 &= ABC + AB\bar{C} + A\bar{B}C + \bar{A}BC + \bar{A}\bar{B}C \\
 &= \sum m(1, 3, 5, 6, 7)
 \end{aligned}$$




⇒ Design Half Adder using only NAND gates.

Sol:-

 

⇒ Design Half Adder using only NOR gates.

Sol:-


 


* Design Full Adder using only

i) NAND gates



ii) NOR gates.

Sol:- (i)

  


* Design Half subtractor using only i) NAND ii) NOR.

Sol:- i)

  


* Design Full subtractor using only i) NAND ii) NOR.

Sol:- i)

 


ii)

 


* Implement the following Boolean function $Y(A, B, C) = AB + C$ using only

- i) NAND gates ii) NOR gates.



Sol:-

 

(ii)

 

ii) $Y(A, B, C) = (A + C)(B + C)$.

  

Note:-

